

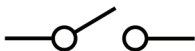







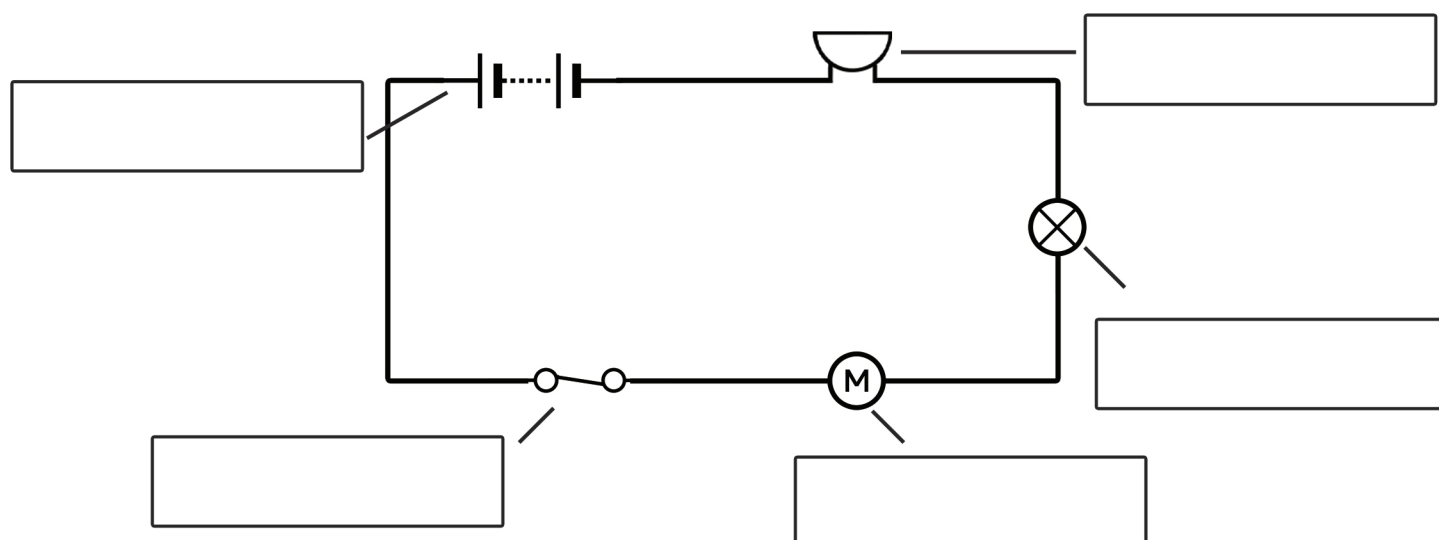


# Electric Circuits

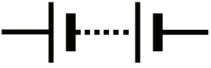

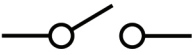
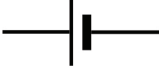






Label the circuit below.

				
battery	closed switch	open switch	cell	voltmeter
				
buzzer	lamp	lamp	motor	wire



# Electric Circuits - Answers

Label the circuit below.

 battery	 closed switch	 open switch	 cell	 voltmeter
 buzzer	 lamp	 lamp	 motor	 wire

